

Digital Logic Circuits 'Combinational Logic'

ELEC2200
Summer 2009

David J. Broderick

brodedj@auburn.edu

<http://www.auburn.edu/~brodedj>

Office: Broun 360



Boolean Algebra Examples

- $\overline{A+B \cdot C}$
- $=\overline{A} \cdot \overline{B \cdot C}$ (DeMorgan's)
- $=\overline{A} \cdot (\overline{B} + \overline{C})$ (DeMorgan's)
- $=\overline{A} \cdot \overline{B} + \overline{A} \cdot \overline{C}$ (Distributivity)

- Both expressions are implementations of the same switching function



Boolean Algebra Examples

- $\overline{A \cdot (B + C) + A' \cdot B}$
- $\overline{A \cdot B + A \cdot C + A' \cdot B}$ (Distributivity)
- $\overline{B + A \cdot C}$ (Absorption)
- $\overline{B} \cdot \overline{A} \cdot \overline{C}$ (DeMorgan's)
- $\overline{B} \cdot (\overline{A} + \overline{C})$ (DeMorgan's)
- $\overline{B} \cdot \overline{A} + \overline{B} \cdot \overline{C}$ (Distributivity)



Boolean Algebra Examples

- $A \cdot B \cdot C + \bar{A} \cdot D + \bar{B} \cdot D + C \cdot D$
- $A \cdot B \cdot C + (\bar{A} + \bar{B}) \cdot D + C \cdot D$ (Absorption)
- $A \cdot B \cdot C + \overline{A \cdot B} \cdot D + C \cdot D$ (DeMorgan's)
- $A \cdot B \cdot C + \overline{A \cdot B} \cdot D$ (Consensus)
- $A \cdot B \cdot C + (\bar{A} + \bar{B}) \cdot D$ (DeMorgan's)
- $A \cdot B \cdot C + \bar{A} \cdot \bar{D} + \bar{B} \cdot \bar{D}$ (Absorption)



Boolean Algebra

- Application of Boolean algebra does simplify expressions
- Requires some creativity, some vigilance, and a little luck
- Can a better method be developed?



Algebraic Forms

- Literal: A variable or its inverse

$$A, B, C, \bar{A}, B', \bar{C}$$

- Product term: Two literals joined by an AND

$$A \cdot B, \bar{B} \cdot C, B \cdot \bar{C}, \bar{A} \cdot \bar{C}$$

- Sum term: Two literals joined by an OR

$$A+B, \bar{B}+C, B+\bar{C}, \bar{A}+\bar{C}$$

- Sum of Products(SOP): Multiple product terms joined by ORs

$$A \cdot B + \bar{B} \cdot C + B \cdot \bar{C} + \bar{A} \cdot \bar{C}$$

- Product of Sums(POS): Multiple sum terms joined by ANDs

$$(A+B) \cdot (\bar{B}+C) \cdot (B+\bar{C}) \cdot (\bar{A}+\bar{C})$$



Canonical Algebraic Forms

- Minterm: A product term in which each variable, or its complement, appears exactly once
- Maxterm: A sum term in which each variable, or its complement, appears exactly once
- Canonical SOP: A SOP expressed using only minterms
- Canonical POS: A POS expressed using only maxterms



Canonical Algebraic Forms

- Canonical SOP Example:

$$f(A,B,C)=A \cdot B \cdot C + A \cdot \bar{B} \cdot C + A \cdot B \cdot \bar{C} + \bar{A} \cdot B \cdot \bar{C}$$

- Canonical POS Example:

$$f(A,B,C)=(A+B+C) \cdot (A+\bar{B}+C) \cdot (A+B+\bar{C}) \cdot (\bar{A}+B+\bar{C})$$

- Canonical expressions remove ambiguity in representing a particular switching function
 - There is only one canonical expression of a switching function
- Canonical expressions allow for simplified expression with a familiar form



Canonical Algebraic Forms

- Examining our switching functions ($n=2$) and selecting $f_B(A,B)$ for an example

A	B	f	f	f	f	f	f	f	f	f	f	f	f	f	f	f	f
		0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

- Each input case that produces an output of 1 can be expressed as an individual minterm
- $f_B(A,B) = \bar{A} \cdot \bar{B} + \bar{A} \cdot B + A \cdot B$
- $f_B(A,B) = \sum m(0, 1, 3)$



Canonical Algebraic Forms

- $f_B(A,B) = \bar{A} \cdot \bar{B} + \bar{A} \cdot B + A \cdot B$

A	B	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot B$	$A \cdot B$	$\bar{A} \cdot \bar{B} + \bar{A} \cdot B + A \cdot B$
0	0	1	1	1	0	0	1
0	1	1	0	0	1	0	1
1	0	0	1	0	0	0	0
1	1	0	0	0	0	1	1



Canonical Algebraic Forms

- Minterms for $f(A,B,C)$

Row #	Inputs	Minterm #	Minterm
0	000	$m(0)$	$\bar{A} \cdot \bar{B} \cdot \bar{C}$
1	001	$m(1)$	$\bar{A} \cdot \bar{B} \cdot C$
2	010	$m(2)$	$\bar{A} \cdot B \cdot \bar{C}$
3	011	$m(3)$	$\bar{A} \cdot B \cdot C$
4	100	$m(4)$	$A \cdot \bar{B} \cdot \bar{C}$
5	101	$m(5)$	$A \cdot \bar{B} \cdot C$
6	110	$m(6)$	$A \cdot B \cdot \bar{C}$
7	111	$m(7)$	$A \cdot B \cdot C$



Canonical Algebraic Forms

- Examining our switching functions ($n=2$) and selecting $f_2(A,B)$ for an example

A	B	f	f	f	f	f	f	f	f	f	f	f	f	f	f	f	f
		0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

- Each input case that produces an output of 0 can be expressed as an individual maxterm
- $f_2(A,B) = (A+B) \cdot (\bar{A}+B) \cdot (\bar{A}+\bar{B})$
- $f_2(A,B) = \Pi M(0,2,3)$



Canonical Algebraic Forms

- $f_2(A,B) = (A+B) \cdot (\bar{A}+B) \cdot (\bar{A}+\bar{B})$

A	B	\bar{A}	\bar{B}	$A+B$	$\bar{A}+B$	$\bar{A}+\bar{B}$	$(A+B) \cdot (\bar{A}+B) \cdot (\bar{A}+\bar{B})$
0	0	1	1	0	1	1	0
0	1	1	0	1	1	1	1
1	0	0	1	1	0	1	0
1	1	0	0	1	1	0	0



Canonical Algebraic Forms

- Maxterms for $f(A,B,C)$

Row #	Inputs	Maxterm #	Maxterm
0	000	M(0)	$A+B+C$
1	001	M(1)	$A+B+\bar{C}$
2	010	M(2)	$A+\bar{B}+C$
3	011	M(3)	$A+\bar{B}+\bar{C}$
4	100	M(4)	$\bar{A}+B+C$
5	101	M(5)	$\bar{A}+B+\bar{C}$
6	110	M(6)	$\bar{A}+\bar{B}+C$
7	111	M(7)	$\bar{A}+\bar{B}+\bar{C}$



Canonical Forms

- What is the canonical SOP expression for $f(A,B,C)=\sum m(1,2,5,7)$?
- What is the canonical POS expression for $f(A,B,C)=\prod M(0,3,4,6)$?



Canonical Forms

- What is the canonical SOP expression for $f(A,B,C)=\sum m(1,2,5,7)$?
 - $f(A,B,C)=\bar{A}\cdot\bar{B}\cdot C+\bar{A}\cdot B\cdot\bar{C}+A\cdot\bar{B}\cdot C+A\cdot B\cdot C$
- What is the canonical POS expression for $f(A,B,C)=\prod M(0,3,4,6)$?
 - $f(A,B,C)=(A+B+C)\cdot(A+\bar{B}+\bar{C})\cdot(\bar{A}+B+C)\cdot(\bar{A}+\bar{B}+C)$



Minimization

- We have looked at heuristic methods
 - Boolean Algebra
 - May result in suboptimal expression
- Now a look at methodical methods
 - **Karnaugh maps**
 - Quine-McCluskey method
 - Petrick's method
 - Generalized Consensus
 - More consistent, optimal results



Minimization

- Our goal: find an SOP/POS expression that contains the fewest terms and literals for a particular switching function
- Minimum SOP(MSOP): fewest product terms
- Minimum POS(MPOS): fewest sum terms



Karnaugh Maps

- Method of minimization
- Useful for up to 6 variables
- An n-variable K-map has 2^n cells that correspond to the 2^n rows of a truth table
- Arrangement of cells is important
- Output of switching function is then used to fill in cells



Karnaugh Maps

- The 2 variable K-map

A\B	0	1
0	Z_0	Z_1
1	Z_2	Z_3

Row	A	B	Z
0	0	0	Z_0
1	0	1	Z_1
2	1	0	Z_2
3	1	1	Z_3

- Cells are positioned so that adjacent cells correspond to a one-bit change in input



Karnaugh Maps

- 3 variable K-map

ABC	0	1
00	Z_0	Z_1
01	Z_2	Z_3
11	Z_6	Z_7
10	Z_4	Z_5

Row	A	B	C	Z
0	0	0	0	Z_0
1	0	0	1	Z_1
2	0	1	0	Z_2
3	0	1	1	Z_3
4	1	0	0	Z_4
5	1	0	1	Z_5
6	1	1	0	Z_6
7	1	1	1	Z_7

- Note reordering in K-Map
- Note wrapping of 1-bit change



Karnaugh Maps

- 4 variable K-map

AB\CD	00	01	11	10
00	Z_0	Z_1	Z_3	Z_2
01	Z_4	Z_5	Z_7	Z_6
11	Z_{12}	Z_{13}	Z_{15}	Z_{14}
10	Z_8	Z_9	Z_{11}	Z_{10}

5 variable K-map

A=0

BC\DE	00	01	11	10
00	Z_0	Z_1	Z_3	Z_2
01	Z_4	Z_5	Z_7	Z_6
11	Z_{12}	Z_{13}	Z_{15}	Z_{14}
10	Z_8	Z_9	Z_{11}	Z_{10}

A=1

BC\DE	00	01	11	10
00	Z_{16}	Z_{17}	Z_{19}	Z_{18}
01	Z_{20}	Z_{21}	Z_{23}	Z_{22}
11	Z_{28}	Z_{29}	Z_{31}	Z_{30}
10	Z_8	Z_9	Z_{11}	Z_{10}



Karnaugh Maps

- 6 variable K-map

A=0
B=0

CD\EF	00	01	11	10
00	Z ₀	Z ₁	Z ₃	Z ₂
01	Z ₄	Z ₅	Z ₇	Z ₆
11	Z ₁₂	Z ₁₃	Z ₁₅	Z ₁₄
10	Z ₈	Z ₉	Z ₁₁	Z ₁₀

A=0
B=1

CD\EF	00	01	11	10
00	Z ₁₆	Z ₁₇	Z ₁₉	Z ₁₈
01	Z ₂₀	Z ₂₁	Z ₂₃	Z ₂₂
11	Z ₂₈	Z ₂₉	Z ₃₁	Z ₃₀
10	Z ₂₄	Z ₂₅	Z ₂₇	Z ₂₆

A=1
B=1

CD\EF	00	01	11	10
00	Z ₄₈	Z ₄₉	Z ₅₁	Z ₅₀
01	Z ₅₂	Z ₅₃	Z ₅₅	Z ₅₄
11	Z ₆₀	Z ₆₁	Z ₆₃	Z ₆₂
10	Z ₅₆	Z ₅₇	Z ₅₉	Z ₅₈

A=1
B=0

CD\EF	00	01	11	10
00	Z ₃₂	Z ₃₃	Z ₃₅	Z ₃₄
01	Z ₃₆	Z ₃₇	Z ₃₉	Z ₃₈
11	Z ₄₄	Z ₄₅	Z ₄₇	Z ₄₆
10	Z ₄₀	Z ₄₁	Z ₄₃	Z ₄₂



Karnaugh Maps

- Let's populate a K-map

$$f(A,B,C,D)=$$

$$\sum m(1,2,3,6,8,9,10,12,13,14)$$

AB\CD	00	01	11	10
00				
01				
11				
10				

Row	A	B	C	D	Z
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	0



Karnaugh Maps

- Let's populate a K-map

$$f(A,B,C,D)=$$

$$\sum m(1,2,3,6,8,9,10,12,13,14)$$

AB\CD	00	01	11	10
00		1	1	1
01				1
11	1	1		1
10	1	1		1

Row	A	B	C	D	Z
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	0



Karnaugh Maps

- We now group the cells with 1's together

- Taking a simple group:

AB\CD	00	01	11	10
00		1	1	1
01				1
11	1	1		1
10	1	1		1

- The two minterms associated with this group are:

- $\bar{A} \cdot \bar{B} \cdot \bar{C} \cdot D + \bar{A} \cdot \bar{B} \cdot C \cdot D$



Karnaugh Maps

- Recall Shannon's Expansion Theorem
- $f(A,B,C,D) = C \cdot f(A,B,1,D) + \bar{C} \cdot f(A,B,0,D)$
- $\bar{A} \cdot \bar{B} \cdot \bar{C} \cdot D + \bar{A} \cdot \bar{B} \cdot C \cdot D$
- $\bar{C} \cdot \bar{A} \cdot \bar{B} \cdot D + C \cdot \bar{A} \cdot \bar{B} \cdot D$
- $(\bar{C} + C) \cdot \bar{A} \cdot \bar{B} \cdot D$
- $\bar{A} \cdot \bar{B} \cdot D$
- This is minimal product term for this group

AB\CD	00	01	11	10
00		1	1	1
01				1
11	1	1		1
10	1	1		1



Karnaugh Maps

- Applying this to other groups

- $\bar{A} \cdot \bar{B} \cdot C \cdot \bar{D} + \bar{A} \cdot B \cdot C \cdot \bar{D}$

- $\bar{A} \cdot C \cdot \bar{D}$

- $A \cdot B \cdot C \cdot \bar{D} + A \cdot \bar{B} \cdot C \cdot \bar{D}$

- $A \cdot C \cdot \bar{D}$

- $\bar{A} \cdot C \cdot \bar{D} + A \cdot C \cdot \bar{D}$

- $(\bar{A} + A) \cdot C \cdot \bar{D}$

- $C \cdot \bar{D}$ ← Minimal product term for two groups together

AB\CD	00	01	11	10
00		1	1	1
01				1
11	1	1		1
10	1	1		1



Karnaugh Maps

- Rules for grouping K-map cells:
 - Groups must contain 2^n cells
 - Groups must be rectangular
 - All cells must contain equivalent values (1,0,d)
 - A group must cover a cell that is not covered by any other group
 - The larger the groups, the simpler the expression
 - Fewer groups results in fewer terms



Karnaugh Maps

- Another look at our example

- 3 groups=3 terms

- $\bar{A} \cdot \bar{B} \cdot D$

- $C \cdot \bar{D}$

- $A \cdot \bar{C}$

- $f(A,B,C,D) = \sum m(1,2,3,6,8,9,10,12,13,14)$

- $f(A,B,C,D) = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot D + \bar{A} \cdot \bar{B} \cdot C \cdot D + \bar{A} \cdot \bar{B} \cdot C \cdot \bar{D} + \bar{A} \cdot B \cdot C \cdot \bar{D} + A \cdot \bar{B} \cdot C \cdot \bar{D} + A \cdot \bar{B} \cdot C \cdot D + A \cdot B \cdot \bar{C} \cdot \bar{D} + A \cdot B \cdot \bar{C} \cdot D + A \cdot B \cdot C \cdot \bar{D} + A \cdot B \cdot C \cdot D$

- $f(A,B,C,D) = \bar{A} \cdot \bar{B} \cdot D + C \cdot \bar{D} + A \cdot \bar{C}$


AB\CD	00	01	11	10
00		1	1	1
01				1
11	1	1		1
10	1	1		1



Karnaugh Maps

- If you can't see the expression corresponding to a group:
- Write all input combinations, order doesn't matter
- If column contains multiple values, cross it out
- Use what's left to form term

AB\CD	00	01	11	10
00		1	1	1
01				1
11	1	1		1
10	1	1		1

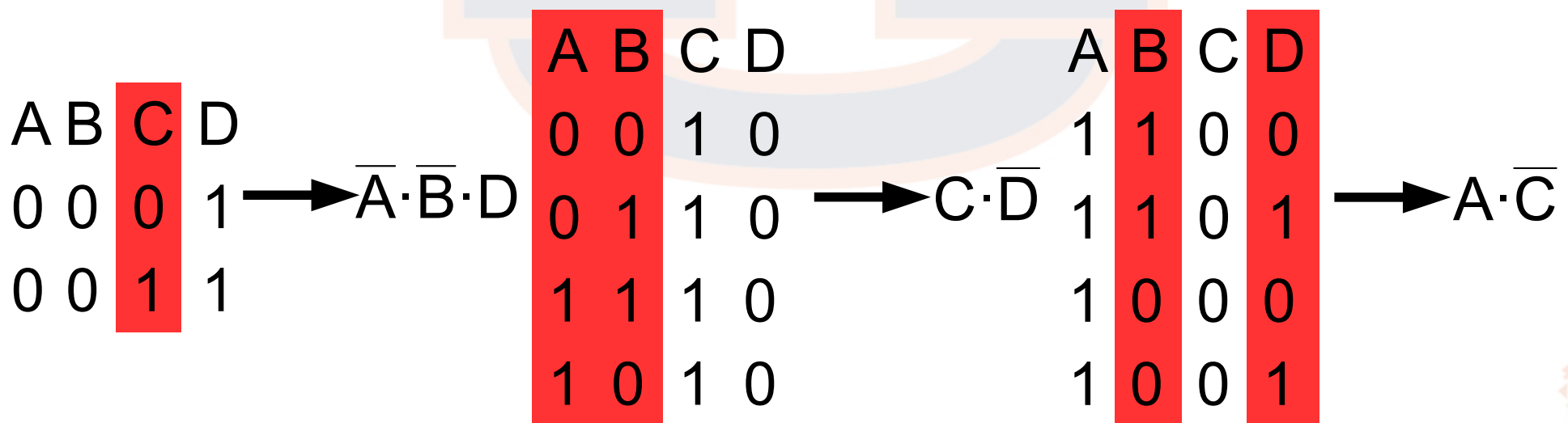

Karnaugh Maps

- We can minimize POS expressions too
- $f(A,B,C,D)=\prod M(0,2,8,10,12,14)$
- Maxterm, fill in zeros

AB\CD	00	01	11	10
00	0			0
01				
11	0			0
10	0			0



Karnaugh Maps

- We can minimize POS expressions too
- $f(A,B,C,D)=\prod M(0,2,8,10,12,14)$
- Worst case, 6 groups

AB\CD	00	01	11	10
00	0			0
01				
11	0			0
10	0			0

- $f(A,B,C,D)=(A+B+C+D) \cdot (A+B+\bar{C}+D) \cdot (\bar{A}+\bar{B}+C+D) \cdot (\bar{A}+B+C+D) \cdot (\bar{A}+\bar{B}+\bar{C}+D) \cdot (\bar{A}+B+\bar{C}+D)$
- This is the canonical POS expression



Karnaugh Maps

- We can minimize POS expressions too
- $f(A,B,C,D)=\prod M(0,2,8,10,12,14)$
- A reasonable guess, 4 groups

AB\CD	00	01	11	10
00	0			0
01				
11	0			0
10	0			0

- $f(A,B,C,D)=(A+B+C+D) \cdot (A+B+\bar{C}+D) \cdot (\bar{A}+C+D) \cdot (\bar{A}+\bar{C}+D)$
- An improvement, but we can do better



Karnaugh Maps

- We can minimize POS expressions too
- $f(A,B,C,D)=\prod M(0,2,8,10,12,14)$
- Remember wrapping, 2 groups!

AB\CD	00	01	11	10
00	0			0
01				
11	0			0
10	0			0

- $f(A,B,C,D)=(B+D)\cdot(\bar{A}+D)$
- This is the MPOS expression



Karnaugh Map

- All expressions implement the same switching function
- $f(A,B,C,D)=(A+B+C+D)\cdot(A+B+\bar{C}+D)\cdot(\bar{A}+\bar{B}+C+D)\cdot(\bar{A}+B+C+D)\cdot(\bar{A}+\bar{B}+\bar{C}+D)\cdot(\bar{A}+B+\bar{C}+D)$
- $f(A,B,C,D)=(A+B+C+D)\cdot(A+B+\bar{C}+D)\cdot(\bar{A}+C+D)\cdot(\bar{A}+\bar{C}+D)$
- $f(A,B,C,D)=(B+D)\cdot(\bar{A}+D)$
- Simplicity=Lower cost, faster response, smaller circuit, etc...
- We'll define these metrics more formally shortly



It's Okay to Not Care

- Sometimes input combinations are of no concern
 - They may not exist.
 - BCD uses only 10 of 16 possible inputs
- If we don't care, output can be either a 1 or a 0
- We can choose whichever one results in the simplest expression



'Don't Cares'

- How do we denote a don't care condition
 - Minterm: $f(A,B,C)=\sum m(1,3,6,7)+d(2)$
 - Maxterm: $f(A,B,C)=\prod M(0,4,5)+d(2)$
- In truth tables and K-maps
 - x,d,-,2 represent a don't care condition
 - x is probably most common
- Let's look at the minterm expression



'Don't Care'

- $Z=f(A,B,C)=\sum m(1,3,6,7)+d(2)$

A	B	C	Z
0	0	0	
0	0	1	1
0	1	0	x
0	1	1	1
1	0	0	
1	0	1	
1	1	0	1
1	1	1	1

A\BC	00	01	11	10
0		1	1	x
1			1	1



'Don't Care'

- If we don't use don't care condition

- $\bar{A} \cdot C + A \cdot B$

- Two terms

- 4 literals

A\BC	00	01	11	10
0		1	1	x
1			1	1

- If we include the don't care cell

- $\bar{A} \cdot C + B$

- Still two terms



- 3 literals

A\BC	00	01	11	10
0		1	1	x
1			1	1




BCD \rightarrow 7 Segment

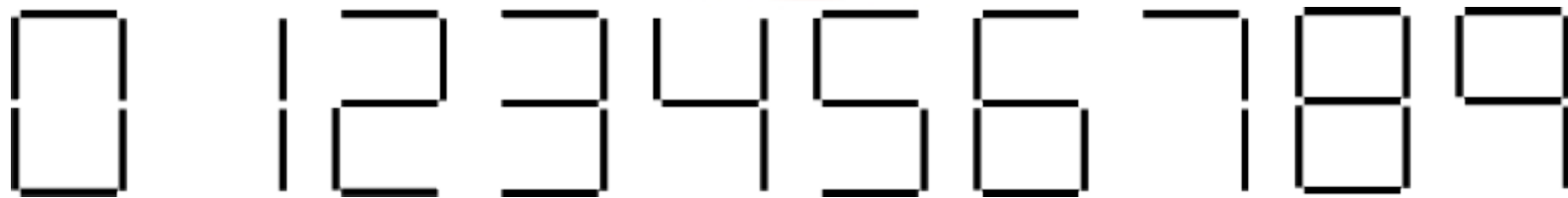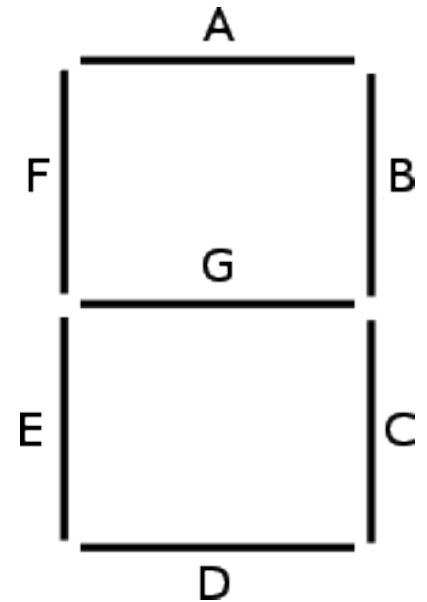- Common Display Method
- A segment is 'on' if a '1' is present
- 4 inputs (BCD value)
- 7 outputs (Segment value)
- 7 individual expressions





BCD \rightarrow 7 Segment

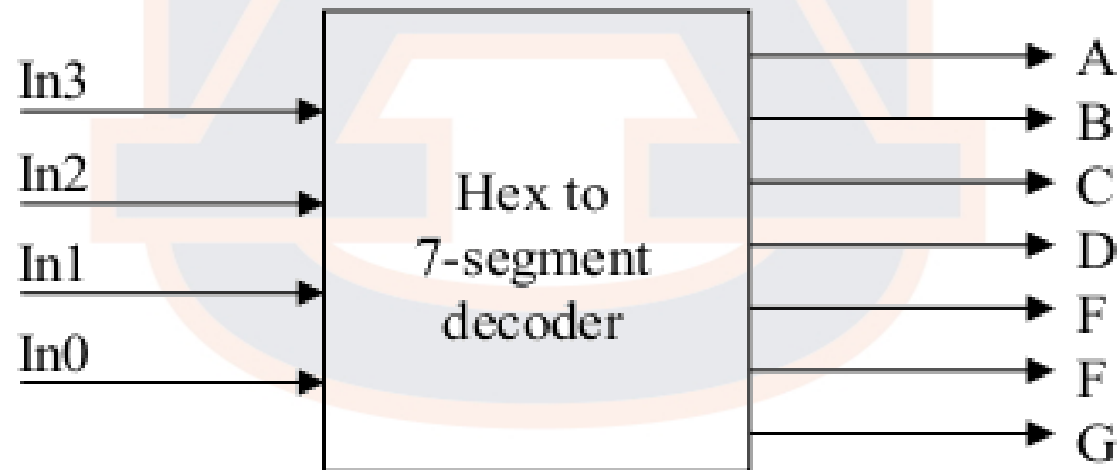- All inputs shared by all 7 circuits
- Each circuit \rightarrow One truth table column
- Each circuit \rightarrow One K-map



BCD → 7 Segment

Digit	In3	In2	In1	In0	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
A	1	0	1	0	x	x	x	x	x	x	x
B	1	0	1	1	x	x	x	x	x	x	x
C	1	1	0	0	x	x	x	x	x	x	x
D	1	1	0	1	x	x	x	x	x	x	x
E	1	1	1	0	x	x	x	x	x	x	x
F	1	1	1	1	x	x	x	x	x	x	x

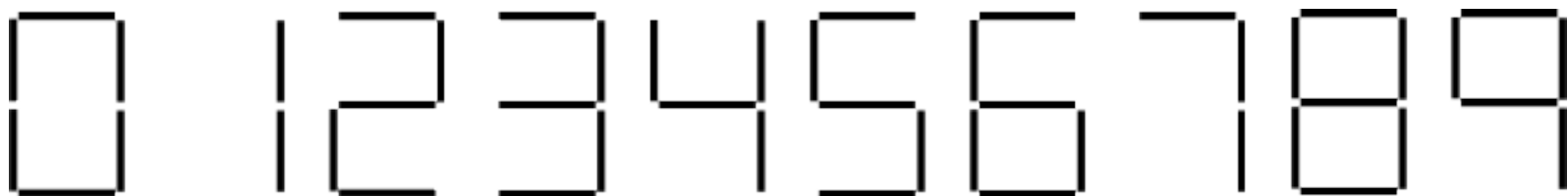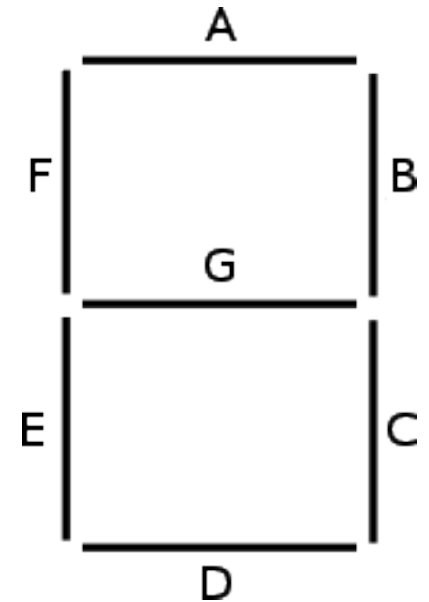

BCD \rightarrow 7 Segment

- After we have expressions we must
 - Draw logic diagram
 - Analyze size and performance
 - Simulate for design validation
 - Optimize
 - Re-simulate optimized desing

